



## INSTITUTE OF AERONAUTICAL ENGINEERING (Autonomous)

Four Year B.Tech III Semester End Examinations (Supplementary) - July, 2018

**Regulation: IARE – R16**

### ELECTRONIC DEVICES AND CIRCUITS

**Time: 3 Hours**

**(Common to ECE | EEE )**

**Max Marks: 70**

**Answer ONE Question from each Unit**

**All Questions Carry Equal Marks**

**All parts of the question must be answered in one place only**

#### **UNIT – I**

1. (a) Explain the static and dynamic resistance of a diode with relevant expressions. Illustrate the two breakdown mechanisms in a diode with relevant example and figure. [7M]
- (b) Determine the germanium PN junction diode current for the forward bias voltage of 0.2V at room temperature  $24^{\circ}\text{C}$  with reverse saturation current equal to 1.1mA. Take  $\eta = 1$  [7M]
2. (a) What is a Zener diode? Explain the construction, working and VI characteristics of Zener diode. Illustrate how Zener diode is used a voltage regulator with example and relevant figure [7M]
- (b) Determine the forward resistance of a silicon PN junction diode when the forward current is 5 mA at room temperature. [7M]

#### **UNIT – II**

3. (a) Calculate the ripple factor for the half wave rectifier with a shunt capacitor filter. [7M]
- (b) A half wave rectifier is used to supply 24V D.C power to a resistive load of  $500\Omega$  and the diode has a forward resistance of  $50\Omega$ . Calculate the maximum value of the A.C. voltage required at the input. [7M]
4. (a) A full-wave rectifier is connected with capacitive filter. Derive expression for the ripple factor and draw relevant waveforms [7M]
- (b) A full wave rectifier has a center tapped transformer 100-0-100 V. Each one of the diode is rated at  $I_{\text{max}}$  of 400 mA and  $I_{\text{av}}$  of 150 mA. Neglecting the voltage drop across the diodes, find
  - i. The value of the load resistance that give the largest DC power output [7M]
  - ii. DC output voltage
  - iii. DC load current and
  - iv. PIV of each diode

#### **UNIT – III**

5. (a) Highlight the need and importance of JFET. Compare the salient features of JFET and bipolar junction transistor(BJT). [7M]
- (b) Compare and contrast JFET with MOSFET? Draw the symbols of MOSFETs. [7M]

6. (a) Illustrate the common base configuration of BJT with relevant figures and explain its input and output characteristics. [7M]
- (b) A transistor operating in CB configuration has  $I_C = 2.98\text{mA}$ ,  $I_E = 3.0\text{mA}$  and  $I_{co} = 0.01\text{mA}$ . What current will flow in collector circuit of that transistor when connected in CE configuration and base current is  $30\mu\text{A}$  [7M]

## UNIT – IV

7. (a) Explain the two important factors to be considered while designing the biasing circuit which are responsible for shifting the operating point. Also list the requirements of a biasing circuit. [7M]
- (b) Explain the construction and operation of N-channel enhancement type MOSFET with the help of its(ID-VDS) and (ID-VGS) characteristics. [7M]
8. (a) Discuss the need to fix the operating point of a transistor and illustrate the DC load line analysis of common emitter output characteristics of BJT. [7M]
- (b) A collector to base circuit shown in Figure 1 has  $V_{CC} = 24\text{ V}$ ,  $R_B = 180\text{ K}\Omega$ ,  $R_C = 3.3\text{ K}\Omega$  and  $V_{CE} = 10\text{ V}$ . Calculate  $h_{FE}$ . Determine  $V_{CE}$  when a new transistor is replaced having  $h_{FE} = 120$  [7M]

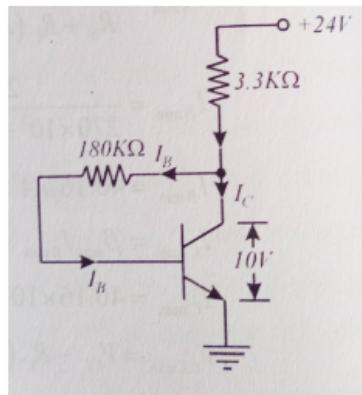


Figure 1

## UNIT – V

9. (a) Draw the small signal equivalent circuit of the source follower circuit and derive the equations for voltage gain, input admittance and output admittance. [7M]
- (b) For the circuit shown in Figure 2 below,  $V_{CC} = 20\text{ V}$ ,  $R_C = 2\text{ k}\Omega$ ,  $\beta = 50$ ,  $V_{BEact} = 0.2\text{ V}$ ,  $R_1 = 100\text{ k}\Omega$ ,  $R_2 = 5\text{ k}\Omega$  and  $R_E = 100\Omega$ . Calculate  $I_B$ ,  $V_{CE}$  and  $I_C$ . [7M]

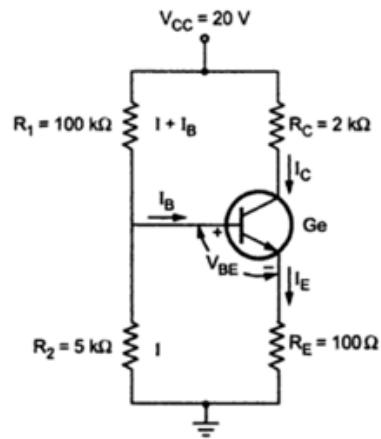


Figure 2

10. (a) Classify the amplifiers based on biasing conditions. [7M]  
 (b) In the common gate amplifier,  $R_D = 2\text{ K}\Omega$ ,  $gm = 1.43 \times 10^{-3}\text{ mho}$  and  $r_d = 35\text{ K}\Omega$ . Evaluate the voltage gain  $AV$ . [7M]

— o o ○ o o —