

--	--	--	--	--	--	--	--	--	--



INSTITUTE OF AERONAUTICAL ENGINEERING

(Autonomous)

B.Tech III Semester End Examinations (Regular) - December, 2017

Regulation: IARE – R16

DIGITAL SYSTEM DESIGN (Electronics and Communication Engineering))

Time: 3 Hours

Max Marks: 70

Answer ONE Question from each Unit

All Questions Carry Equal Marks

All parts of the question must be answered in one place only

UNIT – I

1. (a) Perform the following. [7M]
 - i. $(988.85)_{10} = (?)_{16} = (?)_2$
 - ii. $(11101010.01011)_2 = (?)_{10} = (?)_{16}$
- (b) Distinguish between weighted and non-weighted codes with suitable example. [7M]
2. (a) Generate a 7 bit odd parity Hamming Code for the given 4 bit data word 1101. [7M]
- (b) Perform the following. [7M]
 - i) $10101001-10010011$ using 2's complement method
 - ii) $(650)-(335)$ BCD subtraction using 9's complement method.

UNIT – II

3. (a) Discuss the properties of Boolean algebra. [7M]
- (b) Design the combinational logic circuit to convert BCD code to Excess-3 code and draw the circuit diagram using minimum number of NAND gates only. [7M]
4. (a) Define combinational logic circuit. Design 3-bit parity generator/checker (output is high for odd number of inputs and low for even number of inputs) using NOR gates only. [7M]
- (b) Use Quine-Mcluskey minimization technique, obtain the minimal sum expression for the Boolean function $f(a, b, c, d) = \sum m(6, 7, 9, 10, 13) + \sum d(1, 4, 5, 11, 15)$. [7M]

UNIT – III

5. (a) Write the truth table for a binary full subtractor function and obtain the irredundant disjunctive normal expressions for the function. Show how the function could be realized using minimum number of NAND gates. [7M]
- (b) Design 4-bit carry look ahead adder network and write its important merits. [7M]
6. (a) Design an EX-OR and EX-NOR Gate using NAND Gates [7M]
- (b) Describe the 4-bit serial adder using full adder with block diagram and illustrate with example. [7M]

UNIT – IV

7. (a) Explain the operation of Master slave JKFF using logic circuit, function table and timing diagram. [7M]
- (b) Draw the logic diagram for 4-bit universal shift register to perform the following operations, illustrate this register operation with suitable example. [7M]

MODE s1 s0	OPERATION
0 0	Hold
0 1	Shift Left
1 0	Shift Right
1 1	Parallel Load

8. (a) State and Derive the characteristic equations for TFF, SRFF and JKFF. [7M]
- (b) Design a MOD-5 Synchronous counter using clocked D-FF for the sequence 0, 4, 1, 2, 3, 0, 4, [7M]

UNIT – V

9. (a) Design Mealy sequential network for the following sequence, output is high for non zero present state when input $x = 0$ using edge triggered JKFF. $0 \rightarrow 1 \rightarrow 2$ for $x = 0$, $0 \rightarrow 2 \rightarrow 1$ for $x = 1$. [7M]
- (b) Construct the excitation table, transition table, state table and state diagram for the Moore sequential circuit expression [7M]
 $J_A = B$, $K_A = BX$, $J_B = X$, $K_B = A \oplus X$ and output $Y = A \oplus B$.
10. (a) Describe Mealy and Moore sequential circuit models with neat block diagrams. Compare. [7M]
- (b) Design a Moore type sequence detector to detect a serial input sequence of 101. [7M]

- o o ○ o o -