

--	--	--	--	--	--	--	--	--	--



INSTITUTE OF AERONAUTICAL ENGINEERING

(Autonomous)

B.Tech IV Semester End Examinations (Regular) - May, 2018

Regulation: IARE – R16

Electronic Circuit Analysis

(ECE)

Time: 3 Hours

Max Marks: 70

Answer ONE Question from each Unit

All Questions Carry Equal Marks

All parts of the question must be answered in one place only

UNIT – I

1. (a) Design an emitter follower having $R_i = 600 \text{ k}\Omega$, $R_o = 10 \Omega$. Assume $h_{fe} = 150$, $h_{ie} = 1 \text{ k}\Omega$, $h_{oe} = 25 \mu\text{A/V}$. Find A_I , A_V for the emitter follower using h-parameters. [7M]
- (b) Define h-parameters of CE configuration from the input and output characteristics. [7M]
2. (a) Derive the expression for voltage gain, input and output impedance of a common emitter configuration with neat circuit diagram? [7M]
- (b) Derive the expressions for voltage gain, current gain, input impedance, and output admittance of a common collector amplifier? [7M]

UNIT – II

3. (a) Draw the high frequency equivalent of CE mode amplifier [7M]
- (b) Derive the expression for gain at upper 3dB frequency f_H and discuss the effect of bypass & coupling capacitance. [7M]
4. (a) Derive an expression for short circuit current gain of a transistor with the help of hybrid- π model. [7M]
- (b) Explain the variation of hybrid- π parameters with I_C , V_{CE} and temperature. [7M]

UNIT – III

5. (a) It is desirable to increase the current gain, suggest the suitable multi transistor configuration to boost A_I and derive the expression for A_I with the help of small signal equivalent circuit. [7M]
- (b) Bring out the differences between cascade and cascode type of amplifiers. [7M]
6. (a) Draw the circuit diagram of Darlington configuration and derive the expressions for input, output impedance, voltage and current gains? [7M]
- (b) Calculate overall cut off frequency of 5 stage cascaded amplifiers having single stage lower cut off frequency of 5k Hz. [7M]

UNIT – IV

7. (a) With the help of equivalent circuit, derive the expression for input and output resistance of current shunt feedback amplifier. [7M]
- (b) An amplifier with a closed loop gain of 200 is required and this gain should not vary more than 1 when the inherent gain of the amplifier without feedback varies by 20. Find the values of A_v and β . [7M]
8. (a) Explain how oscillators are classified and conditions for oscillations. [7M]
- (b) Write a short note on [7M]
- Colpitts and Hartley Oscillator
 - RC phase shift Oscillator

UNIT – V

9. (a) Explain the operation of class B push pull amplifier and also derive the expression for maximum conversion efficiency. [7M]
- (b) A single stage class A amplifier has $V_{CC}=20V$, $V_{CEQ}=10V$, $I_{CQ}=600mA$ and collector load resistor $R_L=16\Omega$. The AC output current varies by $\pm 300mA$ with the ac input signal. Determine
- The power supplied by the DC source to the amplifier circuit. [7M]
 - DC power consumed by the load resistor
 - AC power developed across the load resistor
 - DC power delivered to the transistor
 - DC power wasted in transistor collector
 - Overall efficiency
10. (a) Explain the operation of transformer coupled class A amplifier and derive the maximum conversion efficiency. [7M]
- (b) Briefly discuss the operation of class 'B' amplifier and uses. [7M]

— o o ○ o o —