

--	--	--	--	--	--	--	--	--	--



INSTITUTE OF AERONAUTICAL ENGINEERING

(Autonomous)

B.Tech III Semester End Examinations (Regular) - December, 2017

Regulation: IARE – R16

NETWORK ANALYSIS

(Electrical and Electronics Engineering)

Time: 3 Hours

Max Marks: 70

Answer ONE Question from each Unit

All Questions Carry Equal Marks

All parts of the question must be answered in one place only

UNIT – I

1. (a) Derive the equation for the voltage and current in star system. [7M]
 (b) A symmetrical three phase, three wire 440 V supply is connected to a star connected load. The impedance in each branch are $Z_R = 2+j3 \Omega$, $Z_Y = 1-j2 \Omega$ and $Z_B = 3+j4 \Omega$. Find its equivalent delta connected load. The phase sequence is RYB? [7M]

2. (a) The readings of the two wattmeters used to measure power in a capacitive load are -3000 W and 8000 W respectively. Calculate [7M]
 - i. the input power,
 - ii. the power factor at the load. Assume RYB sequence.

- (b) A 400 V, three phase supply feeds an unbalanced three-wire, star connected load. The branch impedances of the load are $Z_R = 4+j8 \Omega$; $Z_Y = 3+j4 \Omega$ and $Z_B = 15+j20 \Omega$. Find the line currents and voltage across each phase impedance. Assume RYB phase sequence. [7M]

UNIT – II

3. (a) In the circuit shown in Figure 1, determine the complete solution for the current, when switch S is closed at $t=0$. Applied voltage is $v(t) = 100 \cos(10^3 t + \pi/2)$. Resistance $R = 20 \Omega$ and inductance $L = 0.1 \text{ H}$. [7M]

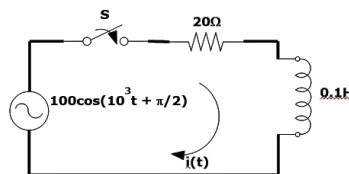


Figure 1

- (b) A series RC circuit consists of a resistor of $10\ \Omega$ and a capacitor of $0.1\ \text{F}$ as shown in Figure 2. A constant voltage of $20\ \text{V}$ is applied to the circuit at $t = 0$. Obtain the current equation. Determine the voltages across the resistor and the capacitor. [7M]

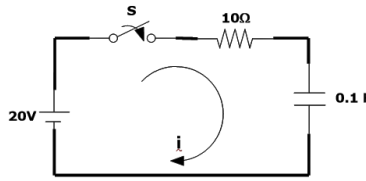


Figure 2

4. (a) A series RLC circuit shown in Figure 3, comprising $R = 10\ \Omega$, $L = 0.5\ \text{H}$ and $C = 1\ \mu\text{F}$ is excited by a constant voltage source of $100\ \text{V}$. Obtain the expression for the current. Assume that the circuit is relaxed initially. [7M]

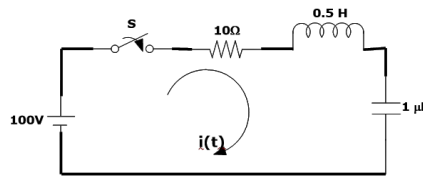


Figure 3

- (b) The circuit shown in Figure 4, consists of series RL elements with $R = 150\ \Omega$ and $L = 0.5\ \text{H}$. the switch is closed when $\phi = 30^\circ$. Determine the resultant current when voltage $V = 50 \cos (100t + \phi)$ is applied to the circuit at $\phi = 30^\circ$? [7M]

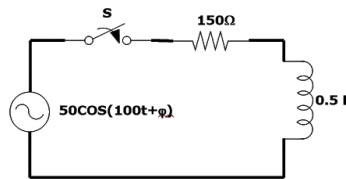


Figure 4

UNIT – III

5. (a) For the circuit shown in Figure 5 plot the locus of the current, mark the range of I for maximum and minimum values of R , and the maximum power consumed in the circuit. Assume $X_L = 25\ \Omega$ and $R = 50\ \Omega$. The voltage is $200\ \text{V}$, $50\ \text{Hz}$. [6M]

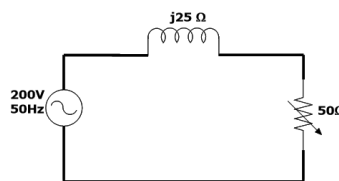


Figure 5

- (b) Obtain the transform impedance of the network shown in Figure 6. [8M]

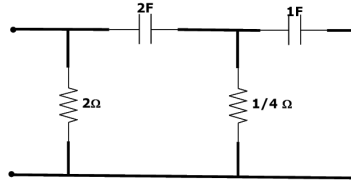


Figure 6

6. (a) List out the necessary conditions for a driving point function. [7M]
 (b) Plot the current locus for the circuit with $R = 50 \text{ Ohms}$ and $X_L = 25 \text{ Ohms}$ variable $V = 200 \text{ V}$, 50 Hz . Find the power consumed. [7M]

UNIT – IV

7. (a) Determine Y parameters in terms of Z parameters. [7M]
 (b) Find the Z parameters for the network shown in Figure 7. [7M]

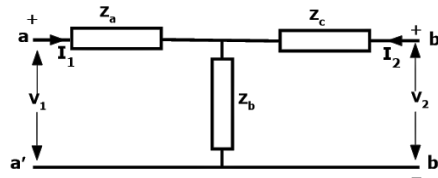


Figure 7

8. (a) Determine the interrelationship between ABCD parameters and Z parameters. [7M]
 (b) Determine ABCD parameters for the following network shown in Figure 8. [7M]

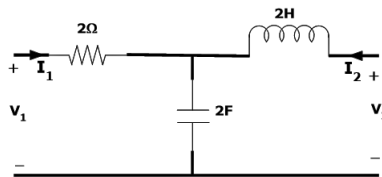


Figure 8

UNIT – V

9. (a) What are the classifications of filter? Discuss them briefly. [7M]
 (b) Design a low pass filter (both π and T section) having a cut off frequency of 2 kHz to operate with a terminated load resistance of $500 \text{ } \Omega$. [7M]
10. (a) Explain briefly about Band Elimination Filter. [7M]
 (b) Design a band-elimination filter having a design impedance of $600 \text{ } \Omega$ and cut-off frequencies $f_1 = 2 \text{ kHz}$ and $f_2 = 6 \text{ kHz}$.