

--	--	--	--	--	--	--	--	--	--



INSTITUTE OF AERONAUTICAL ENGINEERING

(Autonomous)

B.Tech III Semester End Examinations (Supplementary) - February, 2018

Regulation: IARE – R16

NETWORK ANALYSIS

(Electrical and Electronics Engineering)

Time: 3 Hours

Max Marks: 70

Answer ONE Question from each Unit

All Questions Carry Equal Marks

All parts of the question must be answered in one place only

UNIT – I

1. (a) A three phase, balanced delta connected load of $4+j8 \Omega$ is connected across a 400 V, three phase balanced supply. Determine the phase currents and line currents. Assume the phase sequence to be RYB? [7M]
- (b) Explain in detail the star delta method of solving unbalanced load? [7M]
2. (a) The input power to a three phase load is 10 kW at 0.8 pf. Two wattmeters are connected to measure the power, find the individual readings of the wattmeters? [7M]
- (b) An unbalanced four wire, star connected load has a balanced voltage of 400V, the loads are $Z_1 = 4+j8 \Omega$, $Z_2 = 3+j4 \Omega$ and $Z_3 = 15+j20 \Omega$ Calculate the [7M]
 - (a) Line currents
 - (b) Current in the neutral wire?

UNIT – II

3. (a) In the circuit shown in Figure 1 switch is closed at $t=0+$ Find the value of I, di/dt , d^2i/dt^2 . [7M]

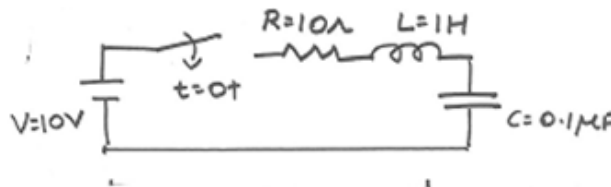


Figure 1

- (b) In the circuit shown in Figure 2, switch is open at $t=0+$. Find the values of V , dv/dt , d^2v/dt^2 . [7M]

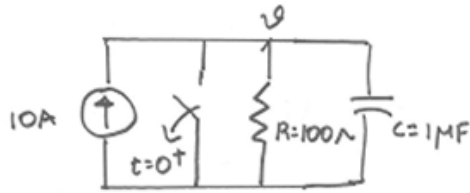


Figure 2

4. (a) Determine the voltage $V(t)$ shown in Figure 3, when the switch is opened at $t=0+$ using Laplace transform method. [7M]

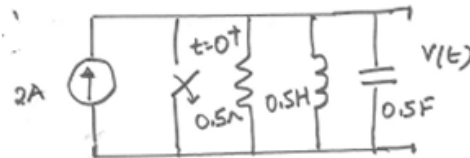


Figure 3

- (b) In the network shown in Figure 4, the switch is opened at $t=0+$. Find the steady state value of $I(t)$ using Laplace transform method. [7M]

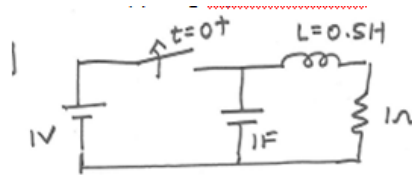


Figure 4

UNIT – III

5. (a) For the circuit shown in Figure 5 if the reactance is variable, plot the range of I for maximum and minimum values of X_L and maximum power consumed in the circuit? [7M]

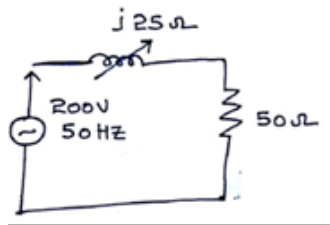


Figure 5

- (b) For the network shown in Figure 6 obtain the transfer functions $G_{21}(S)$ and $Z_{21}(S)$ and the driving point impedance $Z_{11}(S)$? [7M]

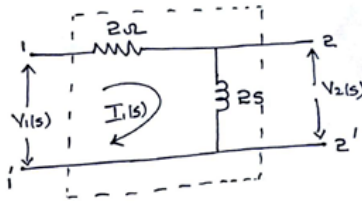


Figure 6

6. (a) Draw the locus diagrams for the following [7M]
- Fixed R and variable L circuit
 - Fixed R and variable C circuit.
- (b) Plot the current locus for the circuit with $R = 50\text{Ohms}$ and $X_c = 25\text{Ohms}$ with variable C. Find the power consumed with a supply voltage of 200V, 50HZ. [7M]

UNIT – IV

7. (a) Determine Y parameters for the following network shown in Figure 7. [7M]

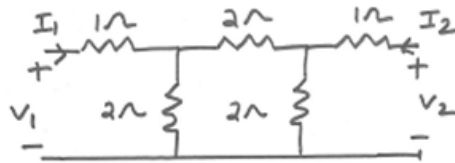


Figure 7

- (b) Determine the transmission(ABCD) parameters in terms of short circuit(Y) parameters. [7M]
8. (a) Two networks are connected in series shown in Figure 8. Obtain the Z-parameters of the combination. Also verify by direct calculation? [7M]

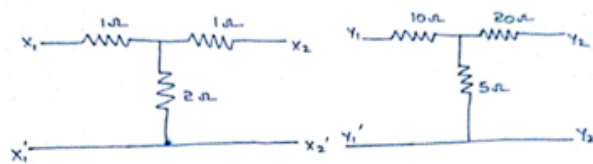


Figure 8

- (b) Find the h-parameters of the network shown in Figure 9? [7M]

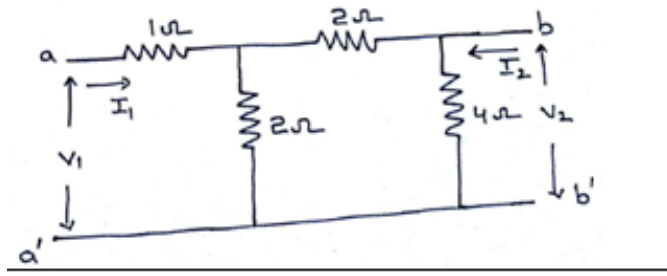


Figure 9

UNIT – V

9. (a) Derive the propagation constant of a symmetrical T network. [7M]
- (b) Design m derived low pass T filter having a cut off frequency of 1kHz, design impedance of 400ohms and resonant frequency of 1100Hz. [7M]
10. (a) Classify the various types of filters and derive the design equations of a K type low pass filter. [7M]
- (b) Design a k type band stop T filter having design impedance of 600ohms and cut off frequency of 2kHz and 6kHz. [7M]

— ○ ○ ○ —