

| | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|
| | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|



INSTITUTE OF AERONAUTICAL ENGINEERING

(Autonomous)

B.Tech III Semester End Examinations (Regular) - December, 2017

Regulation: IARE – R16

DIGITAL LOGIC DESIGN

(Common to CSE / IT)

Time: 3 Hours

Max Marks: 70

Answer ONE Question from each Unit

All Questions Carry Equal Marks

All parts of the question must be answered in one place only

UNIT – I

1. (a) Perform the subtraction with the following decimal numbers by taking the 10's complement of the subtrahend. [6M]
 - i. 20-100
 - ii. 1753-8640
- (b) Convert the decimal 153 to octal and $(0.6875)_{10}$ to binary, clearly indicate each step during the process of conversion. [8M]
2. (a) Illustrate the process of detecting errors during the transmission of information from one location to another using parity bits. [7M]
- (b) What is Radix complement? Explain the procedure of complementing r of an n -digit number N in base r . [7M]

UNIT – II

3. (a) Convert the following expressions into sum of products and product of sums: [5M]
 - i. $(AB+C)(B+C'D)$
 - ii. $x' + x(x+y')(y+z')$
- (b) Simplify the following Boolean functions by first finding the essential prime implicants: [9M]
 - i. $F(w, x, y, z) = \sum m(0,2,4,5,6,7,8,10,13,15)$
 - ii. $F(A, B, C, D) = \sum m(1,3,4,5,10,11,12,13,14,15)$
4. (a) Simplify the following boolean function $F(A,B,C,D,E) = \pi(0,2,4,6,9,13,21,23,25,29,31)$. [7M]
- (b) Simplify the following boolean functions to a minimum number of literals. [7M]
 - i. $x+x'y$
 - ii. $x(x'+y)$
 - iii. $x'y'z+x'yz+xy'$

UNIT – III

5. (a) Implement a full adder circuit using half adder circuits and OR gate. [7M]
- (b) Design a BCD to 2421 Code Converter Circuit. [7M]
6. Realize the following Boolean function using the following MUX [14M]
 $F(A, B, C, D) = \sum m(1, 4, 5, 7, 9, 12, 13)$ using 16X1 MUX and 8X1 MUX

UNIT – IV

7. (a) Explain the characteristics of JK flip-flop with the help of logic diagram, characteristic table and characteristic equation. [7M]
- (b) Explain the design procedure for 3-bit binary counter using T-flip-flop. [7M]
8. (a) Design a BCD Ripple counter using JK Flip Flops. [7M]
- (b) Design a 4 bit Johnson counter with initial value to be 0000 using D Flip flops. [7M]

UNIT – V

9. (a) Using PROM, realize the following expressions [7M]
- $F1(a, b, c) = \sum m(0, 1, 3, 5, 7)$
- $F2(a, b, c) = \sum m(1, 2, 5, 6)$
- (b) Implement the circuit with a PLA [7M]
- $F1(a, b, c) = \sum m(0, 1, 3, 4)$
- $F2(a, b, c) = \sum m(1, 2, 3, 4, 5)$
10. Implement the following Boolean functions given in sum of min terms using PAL [14M]
- $W(A, B, C, D) = \sum m(2, 12, 13)$
- $X(A, B, C, D) = \sum m(7, 8, 9, 10, 11, 12, 13, 14, 15)$
- $Y(A, B, C, D) = \sum m(0, 2, 3, 4, 5, 6, 7, 8, 9, 10, 11, 15)$
- $Z(A, B, C, D) = \sum m(1, 2, 8, 12, 13)$

— o o ○ o o —