

--	--	--	--	--	--	--	--	--	--



INSTITUTE OF AERONAUTICAL ENGINEERING

(Autonomous)

B.Tech III Semester End Examinations (Regular), February – 2021

Regulation: IARE–R18

ANALOG ELECTRONICS

(EEE)

Time: 3 Hours

Max Marks: 70

Answer any Four Questions from Part A

Answer any Five Questions from Part B

PART – A

1. With a neat circuit diagram explain the input and output characteristics of BJT in CC configuration. [5M]
2. Explain the construction of depletion type P-channel MOSFET. [5M]
3. Briefly explain about cascade amplifiers. [5M]
4. Explain in detail about voltage shunt feedback amplifier. [5M]
5. Explain the operation of non-inverting Op-amp. [5M]
6. A transistor employs a 4 kΩ load and $V_{CC} = 13V$. What is the maximum input signal if $\beta = 100$? [5M]
7. Draw the small-signal model of common source FET amplifier. [5M]
8. Draw and explain the operation of an op-amp as differentiator for sine wave input. [5M]

PART – B

9. Explain the operation of PN junction diode under forward and reverse bias conditions and sketch the V-I characteristics. [10M]
10. A p-n-p germanium transistor is used in the self biasing arrangement with $V_{CC} = 5V$, $R_1 = 27k\Omega$, $R_2 = 3k\Omega$, $R_E = 270\Omega$, $R_C = 2k\Omega$, $\beta=50$. Find V_{CEQ} and I_{CQ} . [10M]
11. Draw the small-signal model of common drain FET amplifier. Obtain the expressions for voltage gain and output resistance? [10M]
12. A common drain amplifier uses FET having dynamic drain resistance $r_d = 200$ k-ohm and $\mu = 20$. Calculate the output impedance and voltage gain for following values of load resistor R_s : i) 200 ii) 400 iii) 600 [10M]
13. Explain the two stage amplifier with Darlington connection. What are the drawbacks of a Darlington amplifier? [10M]
14. Draw the circuit diagram of direct coupled class-A power amplifier and explain its operation. Show that the maximum conversion efficiency is 25%. [10M]
15. Determine the expression for frequency oscillation of Hartley oscillator using transistor. [10M]
16. A quartz crystal has the following constants. $L=50mH$, $C_1=0.02pF$, $R=500$ and $C_2=12pF$. Find the values of series and parallel resonant frequencies. If the external capacitance across the crystal changes from 5pF to 6pF, find the change in frequency of oscillations [10M]
17. With a neat diagram explain about square wave generator and determine the frequency of oscillation. [10M]
18. Design an op-amp differentiator that will differentiate an input signal with $f_{max}=100Hz$. Draw the output waveform for sine wave of 1 V peak at 100 Hz applied to the differentiator. Also repeat it for square wave input. [10M]