

**INSTITUTE OF AERONAUTICAL ENGINEERING**

(Autonomous)

(Dundigal-500043, Hyderabad)

**B.Tech III SEMESTER END EXAMINATIONS (REGULAR) - FEBRUARY 2022**

Regulation:UG-20

**ELECTRONIC DEVICES AND CIRCUITS****Time: 3 Hours****(ECE)****Max Marks: 70****Answer ALL questions in Module I and II****Answer ONE out of two questions in Modules III, IV and V**

NOTE: Provision is given to answer TWO questions from among one of the Modules III / IV / V

**All Questions Carry Equal Marks****All parts of the question must be answered in one place only****MODULE – I**

1. (a) Draw the full-wave rectifier with center tapped transformer with relevant waveforms and derive expression for its efficiency. [7M]
- (b) A full wave rectifier has a center tapped transformer 100-0-100 V. Each one of the diode is rated at  $I_{max}$  of 400mA. Neglecting the voltage drop across the diodes. Solve
  - i) Efficiency
  - ii) DC output voltage
  - iii) DC load current
  - iv) PIV of each diode [7M]

**MODULE – II**

2. (a) Describe the working of NPN transistor in common base configuration and draw its input and output characteristics. [7M]
- (b) The reverse leakage current of the transistor when connected in CB configuration is  $0.2 \mu A$  and it is  $18 \mu A$  when the same transistor is connected in CE configuration. Calculate  $\alpha_{dc}$  and  $\beta_{dc}$  of the transistor. (Assume  $I_B = 30mA$ ). [7M]

**MODULE – III**

3. (a) Explain any two bias compensation techniques. Contrast bias stabilization and compensation techniques. [7M]
- (b) The h-parameters of a transistor used in a CE circuit are  $h_{ie} = 1.0 K\Omega$ ,  $h_{re} = 2.0 \times 10^{-4}$ ,  $h_{fe} = 50$  and  $h_{oe} = 25 \mu mhos$ . The load resistor for the transistor is  $1K\Omega$  and source resistance is  $800\Omega$ . Determine the value of  $A_V$ ,  $A_I$ ,  $R_i$ , and  $R_O$ . [7M]
4. (a) Draw the Self bias circuit and derive the stability factor for it along with explanation. [7M]
- (b) The h-parameters of a transistor used in a CB circuit are  $h_{ib} = 22\Omega$ ,  $h_{rb} = 3.0 \times 10^{-4}$ ,  $h_{fb} = -0.98$  and  $h_{ob} = 0.5 \mu mhos$ . The load resistor for the transistor is  $1K\Omega$  and source resistance is  $1200\Omega$ . Determine the value of  $A_V$ ,  $A_I$ ,  $R_i$ , and  $R_O$ ,  $A_{VS}$ ,  $A_{IS}$ . [7M]

## MODULE – IV

5. (a) With a neat constructional diagram explain the operation of n-channel depletion-type MOSFET. [7M]
- (b) A JFET amplifier with a voltage-divider biasing circuit has the following parameters:  $V_P = -2V$ ,  $I_{DSS} = 4mA$ ,  $R_D = 910\Omega$ ,  $R_S = 3K\Omega$ ,  $R_1 = 12M\Omega$ ,  $R_2 = 8.57M\Omega$  and  $V_{DD} = 24V$ . Solve the value of drain current  $I_D$  at the operating point. Verify whether the FET will operate in the pinch-off region. [7M].
6. (a) Explain the parameters trans-conductance  $g_m$ , drain resistance  $r_d$  and amplification factor  $\mu$  of a JFET. Establish a relation between them. [7M]
- (b) The device parameters for an n-Channel JFET  $I_{DSS} = 10mA$ ,  $V_p = -4V$  Calculate the drain current for i)  $V_{GS} = 0$  ii)  $V_{GS} = -1.0V$  iii)  $V_{GS} = -4V$ . [7M]

## MODULE – V

7. (a) Explain the V-I characteristics of Zener diode and analyse Avalanche and Zener breakdown mechanisms. [7M]
- (b) A 5V stabilized power supply is required to be produced from a 12V DC power supply input source. The maximum power rating  $P_Z$  of the zener diode is 2W. Solve :
- i) The maximum current flowing through the zener diode.
  - ii) The minimum value of the series resistor,  $R_S$ .
  - iii) The load current  $I_L$  if a load resistor of  $1k\Omega$  is connected across the zener diode.
  - iv) The zener current  $I_Z$  at full load. [7M]
8. (a) Draw the circuit diagram of SCR and explain its operation along with its characteristics. [7M]
- (b) Calculate voltage gain of the CS JFET amplifier given in the Figure 1.  $g_m = 4mA/V$  and  $R_S = 400\Omega$ . (Assume necessary data) [7M]

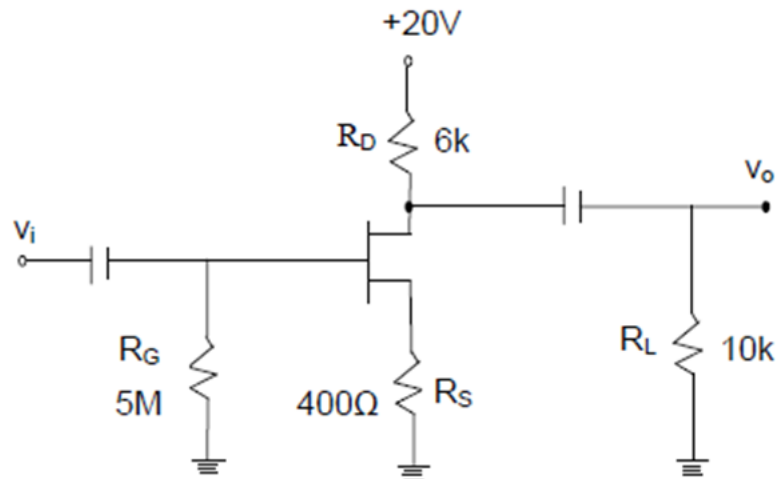


Figure 1

