

# INSTITUTE OF AERONAUTICAL ENGINEERING

(AUTONOMOUS)

Code No: BPE001

## MODEL QUESTION PAPER-2

I M. Tech I Semester Regular Examinations, February 2017

### POWER ELECTRONIC CONTROL OF DC DRIVES

(Power Electronics and Electric Drives)

Time: 3 hours

Max. Marks: 70

Answer ONE Question from each unit

All Questions Carry Equal Marks

All parts of the question must be answered in one place only

.....

#### UNIT – I

- 1 a) Explain the use of freewheeling diode in the converter fed DC drives. Take an example of 1-phase fully controlled converter fed for explanation. How it is going to affect the machine performance. [7M]
- b) A 220V, 1500RPM, 10A separately excited DC Motor has an armature resistance of  $1\Omega$ . It is fed from a single phase full converter with an AC source voltage of 230V, 50Hz. The motor EMF constant is 1.337N-m/A. Assume continuous load current at the firing angle of  $30^\circ$  and torque of 5N- m, calculate the motor speed. [7M]
- 2 a) Describe the operation of single phase fully controlled rectifier control of DC series motor and obtain the expression for motor speed for continuous mode of operation. [7M]
- b) The speed of a 15HP, 220V, 1000RPM DC series motor is controlled using a single-phase half controlled bridge rectifier. The combined armature and field resistance is  $0.2\Omega$ . Assuming continuous and ripple free motor current and speed of 1000 rpm and  $K=0.03$  Nm/Amp determine
  - i. A Motor current
  - ii. Motor torque for a firing angle  $\alpha=30^\circ$  AC source voltage is 250V.[7M]

#### UNIT – II

- 3 a) Explain the motoring and braking operation of three phase fully controlled rectifier control of dc separately excited motor with aid of diagrams and waveforms. Also obtain the expression for motor terminal voltage speed. [7M]
- b) A 600V, 1500RPM, 80A separately excited DC motor is fed through a three-phase semi converter from 3-phase 400 supply. Motor armature resistance is  $1\Omega$  the armature current assumed constant. For a firing angle of  $45^\circ$  at 1200RPM, compute the RMS value of source and thyristor currents, average value of thyristor current and the input supply power factor. [7M]
- 4 a) Explain the operation of three phase half controlled rectifier fed DC separately excited motor drives with waveforms and characteristics. Find out the average, RMS values and the harmonic spectrum of the output voltage / current waveforms of the converter and find out the displacement factor, distortion factor and the power factor of the input current as well as its harmonic spectrum. [7M]
- b) A 230V, 1500RPM, 20A separately excited DC Motor is fed from 3-phase full converter. Motor armature resistance is  $0.6\Omega$ . Full converter is connected to 400V, 50Hz source through a delta-star transformer. Motor terminal voltage is rated when converter firing angle is zero. Calculate the transformer phase turns-ratio from primary to secondary. [7M]

#### UNIT – III

- 5 a) Draw the circuit diagram and explain the operation of closed loop speed control with inner current loop and field weakening. [7M]
- b) A 200V, 1500RPM, 50A separately excited motor with armature resistance of  $0.5\Omega$  is fed from a circulating current dual converter with AC source voltage 165V. Determine converter firing angle for the following operating points [7M]
- Motoring operation at rated motor torque and 1000RPM
  - Braking operation at rated motor torque and 1000RPM.
- 6 a) Distinguish between circulating current and non circulating current mode of operation and their application. [7M]
- b) Speed of a dc series motor coupled to a fan load is controlled by variation of armature voltage. When armature voltage is 400V, motor takes 20A and the fan speed is 250RPM. The combined resistance of armature and field is  $1.0\Omega$ . Calculate [7M]
- Motor armature voltage for the fan speed of 350RPM
  - Motor speed for the armature voltage of 250V.

#### UNIT – IV

- 7 a) Develop the mathematical expression for minimum and maximum currents for a class A chopper operated DC motor with back EMF. [7M]
- b) A chopper used for ON and OFF control of a DC separately excited motor has supply voltage of  $230V_m$ ,  $T_{on} = 10ms$ ,  $T_{off} = 15ms$ . Neglecting armature inductance and assuming continuous conduction of motor current, Calculate the average load current when the motor speed is 1500 rpm, has a voltage constant  $K_v = 0.5V/rad/sec$ . The armature resistance is  $2\Omega$ . [7M]
- 8 a) Explain the operation of chopper for forward motoring and braking control of separately excited DC motor aid of diagram, waveforms and speed torque curves. [7M]
- b) A DC chopper controls the speed of DC series motor. The armature resistance  $R^a = 0.04\Omega$ , field circuit resistance  $R_f = 0.06\Omega$ , and back EMF constant  $K_v = 35M \text{ v/rad/sec}$ . The DC input voltage of the chopper  $V_s = 600V$ . If it is required to maintain a constant developed torque of  $T_d = 547N\cdot m$ , plot the motor speed against the duty cycle K of the chopper. [7M]

#### UNIT – V

- 9 a) Show how can the input current of the rectifier fed booster converter be made sinusoidal and in phase with the input voltage. [7M]
- b) The step up converter has  $R=10\Omega$ ,  $L= 6.5mH$ ,  $E = 5V$  and  $K=0.5$ , find  $I_1$ ,  $I_2$  and  $\Delta I$ . [7M]  
Use SPICE to find these values and plot the load, diode and switch current.
- 10 a) Compute the multi output boost converter be operated with time multiplexing control? [7M]
- b) A DC Regulator is operated at a duty cycle of  $K=0.4$ . The load resistance is  $R=150\Omega$ , the inductor resistance is  $R_L=1\Omega$  and resistance of the filter capacitor is  $R_c=0.2\Omega$ . determine the voltage gain for [7M]
- Buck converter
  - Boost converter and
  - Buck boost converter.