

--	--	--	--	--	--	--	--	--	--



# INSTITUTE OF AERONAUTICAL ENGINEERING

(Autonomous)

B.Tech V Semester End Examinations (Regular) - November, 2018

Regulation: IARE – R16

## INTEGRATED CIRCUITS APPLICATIONS

Time: 3 Hours

(Common to ECE | EEE)

Max Marks: 70

Answer ONE Question from each Unit

All Questions Carry Equal Marks

All parts of the question must be answered in one place only

### UNIT – I

- (a) Define CMRR and derive the expression for CMRR. [7M]

(b) For a dual input, balanced output differential amplifier,  $R_C = 2.2\text{k}\Omega$ ,  $R_E = 4.7\text{k}\Omega$ ,  $R_{S1} = R_{S2} = 50\Omega$ . The supply voltages are  $\pm 10\text{V}$ . the  $h_{fe}$  for the transistor is 50. Assume silicon transistors and  $h_{ie} = 1\text{k}\Omega$ . Determine the operating point values, differential mode gain, common mode gain and CMRR. [7M]
- (a) What is Input Bias Current and explain how can it be reduced? [7M]

(b) With the help of neat diagrams explain about pole zero compensation technique. [7M]

### UNIT – II

- (a) Explain the operation of Log Amplifier using IC741. [7M]

(b) Design an Op-amp circuit to give an output  $V_O = -(3V_1 + 2V_2 + 0.1V_3)$  for  $R_f = 10\text{k}\Omega$  assume necessary data for  $R_1, R_2, R_3$ . [7M]
- (a) Design a Practical differentiator at 2KHz. Assume necessary data for  $R_f$  and  $C_{in}$  [7M]

(b) With the help of neat circuit diagram and waveform explain the operation of Monostable Multi-vibrator using IC741. [7M]

### UNIT – III

- (a) Draw the 1<sup>st</sup> order low pass filter using op-amp and derive the expression for higher cut-off frequency. [7M]

(b) Design a wide band reject filter having  $f_h = 400\text{Hz}$  and  $f_l = 2\text{kHz}$  having pass band gain as 2. Draw the circuit and corresponding frequency response. [7M]

6. (a) With the help of circuit diagram and waveform, explain the working of IC 555 Timer as Monostable multivibrator and derive an expression for pulse width. [7M]  
(b) Design a Notch filter using Op-Amp at 300 Hz. [7M]

#### UNIT – IV

7. (a) Explain the following types of digital to analog converters with suitable circuit diagrams. [7M]  
(i) R-2R Ladder DAC  
(ii) Inverted R-2R DAC  
(b) Draw the circuit diagram for flash type ADC and explain in detail. [7M]
8. (a) Explain the types of digital to analog converters with suitable circuit diagrams for Binary Weighted Resistor DAC. [7M]  
(b) With a neat block diagram explain in detail about successive approximation type analog to digital converter. [7M]

#### UNIT – V

9. (a) Design a 4-bit ripple carry adder and explain its working function. [7M]  
(b) Design a 4-bit synchronous up-down counter using JK flip-flop. [7M]
10. (a) With the help of truth table explain about IC74X85. [7M]  
(b) Explain the operation of 4 bit serial in serial out shift register with the help of functional table. [7M]

– ○ ○ ○ ○ –