

--	--	--	--	--	--	--	--	--	--



# INSTITUTE OF AERONAUTICAL ENGINEERING

(Autonomous)

B.Tech V Semester End Examinations (Supplementary) - January, 2019

Regulation: IARE – R16

## INTEGRATED CIRCUITS APPLICATIONS

Time: 3 Hours

(Common to ECE | EEE)

Max Marks: 70

Answer ONE Question from each Unit

All Questions Carry Equal Marks

All parts of the question must be answered in one place only

### UNIT – I

1. (a) Derive the expression for Q Point, A,  $Z_I$  and  $Z_O$  of a dual input balanced output differential amplifier. [7M]
- (b) Determine the output voltage of the differential amplifier having input Voltages  $V_1=1\text{mV}$  and  $V_2=2\text{ mV}$ . The amplifier has a differential gain of 5000 and CMRR 1000. [7M]
2. (a) Explain the working principle of a BJT differential amplifier with active load. [7M]
- (b) An Op - amp has a slew rate of  $1.5\text{V}/\mu\text{s}$ . What is the maximum frequency of an output sinusoid of peak value 10 V at which the distortion sets in due to the slew rate limitation? [7M]

### UNIT – II

3. (a) With the help of neat diagrams explain the operation of Schmitt Trigger using IC741. [7M]
- (b) In the following Figure 1,  $R_1 = 10\text{ k}\Omega$ ,  $R_f = 100\text{k}\Omega$ ,  $v_i = 1\text{V}$ . A load of  $25\text{ k}\Omega$  is connected to the output terminal. Calculate (i)  $i_1$  (ii)  $v_o$  (iii)  $i_L$  (iv) Total current  $i_0$  into the output pin. [7M]

 


Figure 1

4. (a) Draw the circuit using Op-amp as instrumentation amplifier and explain its working function. [7M]
- (b) In the given circuit shown in Figure 2, let  $R_1 = 5\text{ k}\Omega$ ,  $R_f = 20\text{ k}\Omega$  and  $v_i = 1\text{V}$ . A load resistor of  $5\text{ k}\Omega$  is connected to the output terminal. Calculate [7M]
  - (i)  $v_o$
  - (ii)  $A_{CL}$
  - (iii)  $i_L$
  - (iv) Total current  $i_0$  indicating proper direction of flow.

 


Figure 2

### UNIT – III

5. (a) Draw the block diagram of Phase Locked Loop(PLL) and briefly explain about each block in PLL. [7M]
- (b) Design a wide Band Pass Filter having  $f_l = 400$  Hz,  $f_h = 2$  kHz and pass band gain of 4. Find the value of Q of the filter. [7M]
6. (a) With the help of circuit diagrams and waveform, explain the working of 555 Timer as Astable multivibrator and derive an expression for frequency. [7M]
- (b) Design a Second order Butterworth Low pass filter having upper cut off frequency 2 KHz. Assume necessary data. [7M]

### UNIT – IV

7. (a) What output voltage would be produced by a D/A converter whose output range is 0 to 10 V and whose input binary number is [7M]
  - (i) 10 for a 2-bit D/A Converter
  - (ii) 0110 for a 4-bit D/A Converter
  - (iii) 10111100 for an 8-bit D/A Converter
- (b) With the help of neat circuit diagram and waveform explain the operation of Dual Slope ADC. [7M]
8. (a) Explain voltage mode and current mode operations of R-2R ladder type DAC. [7M]
- (b) A Dual slope ADC uses a 16-bit counter and a 4 MHz clock rate. The maximum input voltage range is +10 V. The maximum integrator output voltage should be -8V when the counter has cycled through  $2^n$  counts. The capacitor used in the integrator is  $0.1\mu\text{F}$ . Find the value of the resistor R of the integrator. [7M]

### UNIT – V

9. (a) What is a carry look ahead adder? Design and implement carry look ahead adder using logical gates. [7M]
- (b) Implement the 4-bit, 8-state Johnson counter using 74x194 and draw the corresponding timing diagram. [7M]
10. (a) Compare synchronous and asynchronous counters. Design 4-bit synchronous counter using T-flip-flops. [7M]
- (b) Implement the parallel input to serial output shift register using 74x163 and 74x166. [7M]