

Fundamentals of Electrical Engineering


Authors

Dr. P Sridhar

Professor and Head
Department of EEE
Institute of Aeronautical Engineering,
Dundigal, Hyderabad, TS-500043

Dr. D Shobha Rani

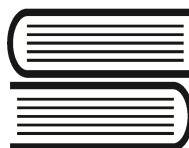Professor
Department of EEE & Controller of Examinations
Institute of Aeronautical Engineering
Dundigal, Hyderabad, TS-500 043



SPECTRUM
UNIVERSITY PRESS

An Innovative Series...

All rights reserved. No part of this publication which is material protected by this copyright notice may be reproduced or transmitted or utilized or stored in any form or by any means now known or hereinafter invented, electronic, digital or mechanical, including photocopying, scanning, recording or by any information storage or retrieval system, without prior written permission from the **Publisher**.

Information contained in this book has been published by **StudentsHelpline Publishing House (P) Ltd. , Hyderabad** and has been obtained by its Authors from sources believed to be reliable and are correct to the best of their knowledge. However, the Publisher and its Authors shall in no event be liable for any errors, omissions or damages arising out of use of this information and specifically disclaim any implied warranties or merchantability or fitness for any particular use.

COPYRIGHT REGISTRATION DIARY NUMBER: 14013/2018-CO/L

Spectrum University Press, Hyderabad

A Part of StudentsHelpline Publishing House (P) Ltd.

(An ISO 9001 : 2015 Certified Company)

Head Office

326/C, 1st Floor, Surneni Nilayam

Near B K Guda Park, S R Nagar, Hyderabad - 500 038, INDIA

P.No:+91 40 23710657, 238000657 Fax: +91 40 23810657

Reg. Off

5-68, Pedda Gorpadu, Pakala, Tirupati, Chittoor - 517 112 AP, INDIA

mail:studentshelpline.in@gmail.com

www:studentshelpline.org

© Spectrum University Press

First Edition-2018

ISBN 978-93-83640-21-8

˘ **280/- Student Edition**

˘ **480/- Library Edition with HB**

Printed at StudentsHelpline Group, S R Nagar, Hyderabad-38

Published by Surneni Mohan Naidu for Spectrum University Press, Hyderabad - 38

Fundamentals of Electrical Engineering

Module-I: Introduction to Electrical Circuits

Circuit Concept: Basic definitions, Ohm's law at constant temperature, classifications of elements, R,L,C parameters, Standard symbols for electrical components, Fuses, independent and dependent sources, Kirchhoff's laws, Equivalent Resistance of series, Parallel and series parallel networks.

Module-II: Analysis of Electrical Circuits

Circuit Analysis: Source Transformation, Star to Delta and Delta to Star transformation, Mesh analysis and Nodal analysis by Kirchhoff's laws, inspection method, super mesh, super node analysis.

Module-III: AC Circuits

Single Phase AC Circuits: Representation of alternating quantities, Instantaneous, peak, RMS, average, form factor and peak factor for different periodic waveforms, phase and phase difference, 'j' notation, Concept of reactance, impedance, susceptance and admittance, rectangular and polar form. Concept of real, reactive, apparent power and complex power, power factor in single phase AC circuits consisting of R, L,C, RL, RC and RLC combinations.

Module-IV: Network Topology

Definitions, Graph, Tree, Incidence Matrix, Basic cut set and Basic Tie set Matrices for Planar Networks, Duality and Dual Networks.

Module-V: Network Theorems

Theorems: Tellegen's, Superposition, Reciprocity, Thevenin's, Norton's, Maximum power transfer and Milliman's and compensation theorems for DC excitations.

Fundamentals of Electrical Engineering

Module-I: Introduction to Electrical Circuits

1.0	Objective and Outcomes	2
1.1	Introduction	2
1.2	Circuit Concept: Basic Definitions	2
1.3	Electric Current	5
1.4	Electric Potential	7
1.5	Potential Difference	7
1.6	Voltage and E.M.F	8
1.7	Power	8
1.8	Ohm's Law at Constant Temperature	8
1.8.1	Limitations of Ohm's Law	9
1.8.2	Applications of Ohm's Law	10
1.8.3	Solved Problems	10
1.9	Classifications of Elements	13
1.10	R-L-C Parameters	14
1.10.1	Resistance (R)	14
1.10.2	Classification of Resistors	16
1.10.3	Colour Coding of Resistors	17
1.11	Inductor (L)	18
1.11.1	Classifications of Inductors	19
1.11.2	Specifications of Inductor	20
1.11.3	Conductivity	20
1.12	Concept of Capacitor	20
1.12.1	Classifications of Capacitors	22
1.12.2	Specifications of the Capacitor	22
1.12.3	Comparison of Active and Passive Components	23
1.12.4	Solved Problems	23

1.13	Standard Symbols for Electrical Components	27
1.14	Fuse	29
1.14.1	Need	30
1.14.2	Rating	30
1.14.3	Requirements of a Fuse	31
1.14.4	Fusing Materials	31
1.14.5	Classification of Fuses	32
1.15	Voltage and Current Sources	35
1.16	Independent and Dependent Sources	36
1.16.1	Solved Problems	39
1.17	Kirchhoff's Laws	39
1.17.1	Solved Problems	43
1.18	Series Resistance	46
1.18.1	Equivalent Resistance for Series Connections	47
1.18.2	Voltage Divider Rule	49
1.18.3	Solved Problems	51
1.19	Resistance in Parallel	55
1.19.1	Characteristics of a Parallel Circuits	57
1.20	Series-Parallel Combination	57
1.21	Division of Current in Parallel Branch Circuit	58
1.21.1	Solved Problems	61
1.21.2	Comparison of Series and Parallel Circuits	64
1.22	Solved Problems on Series and Parallel Circuit	65
1.23	Summary	77
1.24	Review Questions	77
1.25	Multiple Choice Questions	78
Module-II: Analysis of Electrical Circuits		
2.0	Objective and Outcomes	82
2.1	Introduction	82
2.2	Source Transformation	83
2.2.1	Solved Problems	84

2.3	Star to Delta or Delta to Star Transformations	88
2.3.1	Delta-Star Transformation	90
2.3.2	Star-Delta Transformation	91
2.3.3	Conversion of Delta into Equivalent Star	93
2.3.4	Conversion of Star into Equivalent Delta	94
2.3.5	Solved Problems	95
2.4	Mesh Analysis by Kirchhoff's Laws	109
2.5	Node Analysis by Kirchhoff's Laws	122
2.5.1	Concept of Nodal Analysis	122
2.5.2	Nodal Analysis Illustration	123
2.5.3	Solved Problems	124
2.6	Inspection Method	134
2.6.1	Solved Problems	136
2.6.2	Nodal Equations by Inspection Method	137
2.6.3	Solved Problems	138
2.7	Super Mesh for DC Excitations	139
2.7.1	Solved Problems	142
2.8	Super node for DC Excitations	144
2.8.1	Solved Problems	145
2.9	Comparison of Mesh and Nodal Analysis	147
2.10	Summary	149
2.11	Review Questions	149
2.12	Multiple Choice Questions	151
Module-III: AC Circuits		
3.0	Objective and Outcomes	156
3.1	Introduction	156
3.2	Important Definitions	156
3.3	Comparison of Alternating Current and Direct Current	160
3.4	The Sinusoidal Waveform	160
3.4.1	Significance of Sine Wave	162
3.4.2	Different Forms of E.M.F Equation	162

3.5	Representation of Alternating Quantities	162
3.5.1	Instantaneous Values	162
3.5.2	RMS (or) Virtual (or) Effective Value of AC	163
3.5.3	Average (or) Mean Value of AC	165
3.5.4	Form Factor	166
3.5.5	Peak Factor	167
3.5.6	Peak Value (or) Time Period of A.C	167
3.5.7	Solved Problems	168
3.6	Phase Relations	173
3.6.1	Phase	173
3.6.2	Phase Difference	173
3.6.3	Solved Problems	176
3.7	Representation of an AC Quantity by a Rotating Vector	176
3.8	J-operator (or) J Notation	177
3.8.1	Solved Problems	180
3.9	Polar and Rectangular form of Complex Numbers	180
3.10	Phasor Algebra	181
3.11	Impedance Complex Number	182
3.12	Admittance of Complex Number	183
3.13	Concept of Reactance	184
3.14	Impedance	185
3.15	Susceptance	186
3.16	Admittance	186
3.17	Mathematical Representation of Phasors	187
3.18	Solved Problems	189
3.19	Concept of Real, Reactive Power	192
3.20	Apparent Power and Complex Power	194
3.21	Power Factor	195
3.21.1	Solved Problems	196

3.22	AC Circuit	198
3.22.1	AC Through Pure Resistance	198
3.22.2	AC Through Pure Inductance	199
3.22.3	AC Through Capacitance	200
3.23	Representation of AC Series Circuits	201
3.23.1	RL Series Circuit	201
3.23.2	RC Series Circuit	203
3.23.3	RLC Series Circuit	205
3.24	Representation Parallel AC Circuits	208
3.24.1	RL Parallel Circuit	208
3.24.2	RC Parallel Circuit	209
3.24.3	RLC Parallel Circuit	210
3.25	Solved Problems	212
3.26	Advantages of Alternating current over Direct current	221
3.27	Disadvantages of A.C over D.C	222
3.28	Summary	224
3.29	Review Questions	223
3.30	Multiple Choice Questions	225

Module-IV: Network Topology

4.0	Objective and Outcomes	230
4.1	Introduction	230
4.2	Definitions	230
4.3	Graph	235
4.4	Tree	237
4.5	Incidence Matrix	239
4.5.1	Procedure for Constructing Incidence Matrix	239
4.5.2	Properties of Incidence Matrix	239
4.5.3	Solved Problems	241
4.6	Basic Tie set Matrices for Planar Networks	246
4.6.1	Solved Problems	249

4.7	Cut-Set and Tree Branch Voltages	261
4.7.1	Solved Problems	266
4.8	Duality and Dual Networks	276
4.8.1	Solved Problems	280
4.9	Summary	296
4.10	Review Questions	297
4.11	Multiple Choice Questions	298

Module-V: Network Theorems

5.0	Objective and Outcomes	302
5.1	Introduction	302
5.2	Tellegen's Theorem	302
5.2.1	Solved Problems	304
5.3	Superposition Theorem	308
5.3.1	Solved Problems	310
5.4	Reciprocity Theorem	326
5.4.1	Solved Problems	328
5.5	Thevenin's Theorem	338
5.5.1	Solved Problems	341
5.6	Norton's Theorem	353
5.6.1	Solved Problems	355
5.7	Maximum Power Transfer Theorem	369
5.7.1	Solved Problems	371
5.8	Milliman Theorem	378
5.8.1	Solved Problems	380
5.9	Compensation Theorem	383
5.9.1	Solved Problems	385
5.10	Summary	390
5.11	Review Questions	391
5.12	Multiple Choice Questions	394