

# *Electrical Circuits*

## Authors

### **Dr. D. Shobha Rani**

Professor and Controller of Examinations  
Department of EEE  
Institute of Aeronautical Engineering College  
Dundigal, Hyderabad-500043

### **Ms. S. Swathi**

Assistant Professor  
Department of EEE  
Institute of Aeronautical Engineering College  
Dundigal, Hyderabad-500043



**StudentsHelpline® Publishing House (P)Ltd.**

(An ISO 9001:2015 Certified Publisher) *Expect more from us ...*

All rights reserved. No part of this publication which is material protected by this copyright notice may be reproduced or transmitted or utilized or stored in any form or by any means now known or hereinafter invented, electronic, digital or mechanical, including photocopying, scanning, recording or by any information storage or retrieval system, without prior written permission from the **Publisher**.

Information contained in this book has been published by **StudentsHelpline Publishing House (P) Ltd. , Hyderabad** and has been obtained by its Authors from sources believed to be reliable and are correct to the best of their knowledge. However, the Publisher and its Authors shall in no event be liable for any errors, omissions or damages arising out of use of this information and specifically disclaim any implied warranties or merchantability or fitness for any particular use.

**COPYRIGHT REGISTRATION DIARY NUMBER: 5603/2019-CO/L**

### **Head Office**

# 326/C, 1<sup>st</sup> Floor, Surneni Nilayam  
Near B K Guda Park, S R Nagar, Hyderabad - 500 038, INDIA  
P.No:+91 40 23710657, 238000657 Fax: +91 40 23810657

### **Reg. Off**

# 5-68, Pedda Gorpada, Pakala, Tirupati, Chittoor - 517 112 AP, INDIA  
**mail:**studentshelpline.in@gmail.com  
**www:**studentshelpline.in

© StudentsHelpline Publishing House (P) Ltd.

**First Edition–2019**

**ISBN 978-93-83959-61-7**

- ˘ **424/- Student Edition**
- ˘ **624/- Library Edition with HB**

*Printed at M/s StudentsHelpline Group, S R Nagar, Hyderabad-38*

*Published by Surneni Mohan Naidu for StudentsHelpline Publishing House (P) Ltd., Hyderabad - 38*

# *Electrical Circuits*

---

## **Module-I: Introduction to Electrical Circuits**

Circuit Concept: Basic definitions, Ohm's law at constant temperature, classifications of elements, R,L,C parameters, independent and dependent sources, voltage and current relationships for passive elements (for different input signals like square, ramp, saw tooth, triangular and complex), temperature dependence of resistance, tolerance, source transformation, kirchhoff's laws, equivalent resistance of series, parallel and series parallel network.

## **Module-II: Analysis of Electrical Circuits**

Circuit Analysis: Star to Delta and Delta to Star transformation, Mesh analysis and Nodal analysis by Kirchhoff's laws, inspection method, super mesh, super node analysis. Network Topology: Definitions, Incidence Matrix, Basic Tie set and Basic cut set Matrices for Planar Networks, Duality and Dual Networks.

## **Module-III: Single Phase AC Circuits**

Single Phase AC Circuits: Representation of alternating quantities, Instantaneous, peak, RMS, average, form factor and peak factor for different periodic waveforms, phase and phase difference, 'j' notation, Concept of reactance, impedance, susceptance and admittance, rectangular and polar form. Concept of power, real, reactive and complex power, power factor.

Steady state analysis: Steady state analysis of RL, RC and RLC circuits (in series, parallel and series parallel combinations) with sinusoidal excitation; Resonance: series and parallel resonance, concept of band width and Q factor.

## **Module-IV: Magnetic Circuits and Three Phase Circuits**

Magnetic Circuits: Faraday's laws of electromagnetic induction, concept of self and mutual inductance, dot convention, coefficient of coupling, composite magnetic circuit, analysis of series and parallel magnetic circuits. Three Phase Circuits: Star and delta connections, phase sequence, relation between line and phase voltages and currents in balanced systems (both Y &  $\Delta$ ), three phase three wire and three phase four wire systems, analysis of balanced and unbalanced three phase circuits, measurement of active and reactive power.

## **Module-V: Components of Electrical Systems**

Components of Electrical Systems: Switch Fuse Unit (SFU), MCB, ELCB, MCCB, types of wires and cables, Earthing, Types of Batteries: Alkaline battery, Zinc-Carbon battery, dry cell battery, Nickel-Cadmium battery, lead acid battery, lithium ion battery, nickel metal hydride battery, important characteristics for batteries, applications, Elementary calculations for energy consumption.

# *Electrical Circuits*

---

## **Chapter-I: Introduction to Electrical Circuits**

1.0	Objectives	2
1.1	Introduction	2
1.2	Circuit Concept: Basic Definitions	2
1.3	Electric Current	5
1.4	Electric Potential	6
1.5	Potential Difference	7
1.6	Voltage and E.M.F	7
1.7	Power	8
1.8	Ohm's Law at constant temperature	8
1.8.1	Limitations of Ohm's Law	9
1.8.2	Applications of Ohm's Law	9
1.8.3	Solved Problems	9
1.9	Classifications of Elements	12
1.10	R-L-C Parameters	13
1.10.1	Resistance (R)	13
1.10.2	Classification of Resistors	15
1.10.3	Colour Coding of Resistors	16
1.11	Inductor (L)	16
1.11.1	Classifications of Inductors	17
1.11.2	Specifications of Inductor	18
1.11.3	Conductivity	18
1.12	Concept of Capacitor	19
1.12.1	Classifications of Capacitors	20
1.12.2	Specifications of the Capacitor	21
1.12.3	Comparison of Active and Passive Components	21
1.12.4	Solved Problems	22

1.13	Voltage and Current Sources	<b>24</b>
1.14	Independent and Dependent Sources	<b>25</b>
	1.14.1 Solved Problems	<b>27</b>
1.15	Voltage current Relationships for Passive Elements	<b>28</b>
1.16	Temperature Dependence of Resistance	<b>31</b>
1.17	Temperature Co-efficient of Resistance	<b>33</b>
	1.17.1 Expression for Resistance at any Temperature	<b>34</b>
	1.17.2 Formula for Co-efficient of Resistance at any Temperature	<b>35</b>
	1.17.3 Solved Problems	<b>37</b>
1.18	Tolerance	<b>42</b>
	1.18.1 Tolerance in Resistors	<b>42</b>
	1.18.2 Tolerance in Capacitors	<b>45</b>
	1.18.3 Solved Problems	<b>46</b>
1.19	Source Transformation	<b>48</b>
	1.19.1 Solved Problems	<b>49</b>
1.20	Kirchhoff's Law's	<b>53</b>
	1.20.1 Kirchhoff's Current Law	<b>54</b>
	1.20.2 Kirchhoff's Voltage Law	<b>55</b>
	1.20.3 Application of Kirchhoff's Circuit Laws in the Analysis of Circuits	<b>56</b>
	1.20.4 Solved Problems	<b>57</b>
1.21	Series Resistance	<b>62</b>
	1.21.1 Equivalent Resistance for Series Connections	<b>63</b>
	1.21.2 Voltage Divider Rule	<b>65</b>
	1.21.3 Solved Problems	<b>66</b>
1.22	Resistance in Parallel	<b>69</b>
	1.22.1 Characteristics of a Parallel Circuits	<b>71</b>
1.23	Series-Parallel Combination	<b>71</b>
	1.23.1 Division of Current in Parallel Branch Circuit	<b>72</b>
	1.23.2 Comparison of Series and Parallel Circuits	<b>75</b>
	1.23.3 Solved Problems	<b>76</b>
1.24	Summary	<b>88</b>

1.25	Review Questions	<b>89</b>
1.26	Multiple Choice Questions	<b>92</b>
<b>Chapter-II: Analysis of Electrical Circuits</b>		
2.0	Objective	<b>96</b>
2.1	Introduction	<b>96</b>
2.2	Source Transformation	<b>97</b>
	2.2.1 Solved Problems	<b>98</b>
2.3	Star to Delta or Delta to Star Transformations	<b>102</b>
	2.3.1 Delta-Star Transformation	<b>103</b>
	2.3.2 Star-Delta Transformation	<b>105</b>
	2.3.3 Conversion of Delta into Equivalent Star	<b>106</b>
	2.3.4 Conversion of Star into Equivalent Delta	<b>107</b>
	2.3.5 Solved Problems	<b>108</b>
2.4	Mesh Analysis by Kirchhoff's laws	<b>120</b>
2.5	Node Analysis by Kirchhoff's laws	<b>132</b>
	2.5.1 Concept of Nodal Analysis	<b>133</b>
	2.5.2 Nodal Analysis Illustration	<b>133</b>
	2.5.3 Solved Problems	<b>134</b>
2.6	Inspection method	<b>143</b>
	2.6.1 Solved Problems	<b>144</b>
	2.6.2 Nodal Equations by Inspection Method	<b>146</b>
	2.6.3 Solved Problem	<b>147</b>
2.7	Super Mesh for DC Excitations	<b>148</b>
	2.7.1 Solved Problems	<b>151</b>
2.8	Super node for DC Excitations	<b>152</b>
	2.8.1 Solved Problems	<b>153</b>
2.9	Comparison of Mesh and Nodal Analysis	<b>155</b>
2.10	Summary	<b>156</b>
2.11	Review Questions	<b>157</b>
2.12	Multiple Choice Questions	<b>159</b>

### Chapter-III: Network Topology

3.0	Objective	164
3.1	Introduction	164
3.2	Definition	164
3.3	Graph	169
3.4	Tree	171
3.5	Incidence Matrix	173
3.5.1	Procedure for Constructing Incidence Matrix	173
3.5.2	Properties of Incidence Matrix	173
3.5.3	Solved Problems	175
3.6	Basic Tie set Matrices for Planar Networks	180
3.6.1	Solved Problems	183
3.7	Cut-Set and Tree Branch Voltages	194
3.7.1	Solved Problems	199
3.8	Duality and Dual Networks	208
3.8.1	Solved Problems	212
3.9	Summary	229
3.10	Review Questions	229
3.11	Multiple Choice Questions	231

### Chapter-IV: Single Phase AC Circuits

4.0	Objective	236
4.1	Introduction	236
4.2	Important Definitions	236
4.3	Comparison of Alternating Current and Direct Current	240
4.4	The sinusoidal waveform	240
4.4.1	Significance of Sine Wave	242
4.4.2	Different Forms of EMF Equation	242
4.5	Representation of Alternating Quantities	242
4.5.1	Instantaneous Values	242
4.5.2	RMS (or) Virtual (or) Effective Value of AC	243
4.5.3	Average (or) Mean Value of AC	244

4.5.4	Form Factor	246
4.5.5	Peak Factor	246
4.5.6	Peak Value (or) Time Period of A.C	246
4.5.7	Solved Problems	247
4.6	Phase Relations	251
4.6.1	Phase	251
4.6.2	Phase Difference	252
4.6.3	Solved Problems	254
4.7	Representation of an AC Quantity by a Rotating Vector	255
4.8	J-operator (or) J Notation	256
4.8.1	Solved Problems	258
4.9	Polar and rectangular form of Complex Numbers	258
4.10	Phasor Algebra	259
4.11	Impedance Complex Number	260
4.12	Admittance of Complex Number	261
4.13	Concept of Reactance	262
4.14	Impedance	263
4.15	Susceptance	264
4.16	Admittance	264
4.17	Mathematical Representation of Phasors	265
4.18	Solved Problems	266
4.19	Concept of Real, Reactive Power	269
4.20	Apparent Power and Complex Power	270
4.21	Power Factor	272
4.21.1	Solved Problems	273
4.22	AC Circuit	274
4.22.1	AC Through Pure Resistance	274
4.22.2	AC Through Pure Inductance	275
4.22.3	AC Through Capacitance	276
4.23	Representation of AC Series Circuits	277



4.23.1	RL Series Circuit	277
4.23.2	RC Series Circuit	279
4.23.3	RLC Series Circuit	281
4.24	Representation Parallel AC Circuits	283
4.24.1	RL Parallel Circuit	283
4.24.2	RC Parallel Circuit	284
4.24.3	RLC Parallel Circuit	285
4.25	Solved Problems	286
4.26	Advantages of Alternating current over Direct current	293
4.27	Disadvantages of A.C over D.C	294
4.28	Summary	294
4.29	Review questions	295
4.30	Multiple Choice questions	297

### Chapter-V: Resonance

5.0	Objectives	302
5.1	Introduction	302
5.2	Stedy State Concept	302
5.3	Steady state analysis of RL, RC and RLC Series Circuits	303
5.3.1	RL Series Circuit	303
5.3.2	RC Series Circuit	306
5.3.3	RLC Series Circuit	308
5.4	Representation Parallel AC Circuits	310
5.4.1	RL Parallel Circuit	310
5.4.2	RC Parallel Circuit	311
5.4.3	RLC Parallel Circuit	312
5.5	AC parallel circuits	313
5.5.1	Solved Problems	314
5.6	Resonance	328
5.7	Resonance in Series Circuit	329
5.8	Parallel Resonance in RLC Circuit	333
5.9	Q - Factor, Selectivity and Bandwidth	337

5.9.1	Selectivity, Bandwidth and Q-factor of a Series Circuit	337
5.9.2	Selectivity, Bandwidth and Q-factor of Parallel Resonant Circuit	339
5.10	Compare series and parallel resonance circuits	341
5.11	Tank circuit-LC oscillations	342
5.12	Solved Problems	343
5.13	Summary	352
5.14	Review Questions	352
5.15	Multiple Choice Questions	354
<b>Chapter-VI: Magnetic Circuits</b>		
6.0	Objectives	358
6.1	Introduction	358
6.2	Magnetic Circuit	358
6.3	Important definitions	361
6.3.1	Solved Examples	365
6.4	Electro Magnetic Induction	368
6.5	Faraday's Law of Electromagnetic Induction	369
6.5.1	Faraday's First Law	369
6.5.2	Faraday's Second Law	370
6.5.3	Applications of Faraday's Law	370
6.5.4	Integral Form of Faraday's Law	370
6.5.5	Differential Form of Faraday's Law	371
6.5.6	Solved Examples	372
6.6	Direction of Induced E.M.F. and Current	374
6.6.1	Lenz's Law	375
6.6.2	Fleming's Right Hand Rule	376
6.6.3	Fleming's Left-Hand Rule	376
6.7	Induced E.M.F	377
6.7.1	Dynamically Induced E.M.F	377
6.7.2	Statically Induced E.M.F	378
6.8	Motional Electromotive Force	380
6.9	Time Varying Magnetic Fields	381

6.10	Self and Mutual Inductance	<b>382</b>
6.10.1	Self Inductance	<b>382</b>
6.10.2	Mutual Inductance	<b>383</b>
6.10.3	Solved Example	<b>384</b>
6.11	Dot Convention	<b>389</b>
6.11.1	Solved Examples	<b>392</b>
6.12	Co-efficient of coupling	<b>393</b>
6.12.1	Solved Problems	<b>394</b>
6.13	Composite Magnetic Circuit	<b>398</b>
6.14	Analysis of Series and Parallel Magnetic Circuits	<b>401</b>
6.14.1	Analysis of Series Magnetic Circuits	<b>401</b>
6.14.2	Analysis of Parallel Magnetic Circuits	<b>402</b>
6.14.3	Magnetic Leakage (or) Leakage Flux	<b>403</b>
6.14.4	Solved Examples	<b>404</b>
6.15	Comparison between Magnetic and Electric Circuits	<b>417</b>
6.16	Summary	<b>418</b>
6.17	Review Questions	<b>419</b>
6.18	Objective Questions	<b>421</b>
<b>Chapter-VII: Three Phase Circuits</b>		
7.0	Objectives	<b>426</b>
7.1	Introduction	<b>426</b>
7.2	Important Definitions	<b>426</b>
7.3	Three-Phase Circuits	<b>427</b>
7.4	Generation of Three-Phase Voltages	<b>428</b>
7.5	Phase Sequence	<b>430</b>
7.6	Interconnection of Phases	<b>431</b>
7.6.1	Star and Delta Connections	<b>431</b>
7.7	Relation between Line and Phase Voltages and Currents in Balanced System	<b>432</b>
7.7.1	Relationship between Line, Phase Values & Expression for Power for Balanced Star Connection	<b>433</b>

7.7.2	Relationship between Line and Phase Values and Expression for Power for Balanced Delta Connection	435
7.7.3	Comparison between Star and Delta Systems	436
7.7.4	Solved Examples	437
7.8	Advantages of Star and Delta Connected Systems	442
7.9	Three Phase Three Wire and three Phase Four Wire System	442
7.9.1	Three phase three wire systems	442
7.9.2	Three Phase four Wire Systems	444
7.10	Analysis of Balanced Three-Phase Circuits	444
7.10.1	Solved Examples	447
7.11	Analysis of Unbalanced Three Phase Circuits	453
7.11.1	Circulating Current in Unbalanced $\Delta$ -connected Sources	456
7.11.2	Solved Examples	456
7.12	Symmetrical Components	458
7.12.1	Three-phase Circuits with Unbalanced Sources and Balanced Loads	458
7.13	Measurement of Power in 3-Phse Circuits Two Wattmeter Method-Balanced Load	459
7.13.1	Power Factor - Balanced 3-phase load	460
7.13.2	Advantages of Two Wattmeter Method	461
7.13.3	Disadvantages of Two Wattmeter Method	462
7.13.4	Soolved Examples	462
7.14	Summary	472
7.15	Review Questions	472
7.16	Multiple Choice Questions	474
<b>Chapter-VIII: Components of Electrical Systems</b>		
8.0	Objectives	480
8.1	Introduction	480
8.2	Definitions	480
8.3	Fuses	481
8.3.1	Types of Fuses	482
8.3.2	Advantages and Disadvantages of Fuses	483

8.4	Switch Fuse Units	483
8.5	Circuit Breaker	485
8.5.1	The Trip-Circuit	485
8.6	Miniature Circuit Breaker	486
8.6.1	Advantages, Disadvantages and Applications	487
8.7	Earth Leakage Circuit Breaker (ELCB)	488
8.7.1	Advantages and Disadvantages	488
8.8	Moulded Case Circuit Breaker	489
8.8.1	Features	490
8.8.2	Advantages and Disadvantages	490
8.9	Wires and Cables	491
8.9.1	Types of Wires	491
8.9.2	Types of Cables	491
8.10	Earthing	493
8.10.1	Necessity of Earthing	494
8.11	Components of Earthing System	495
8.12	Types of earthing	497
8.13	Advantages of Earthing	501
8.14	Uses of earthing	501
8.15	Batteries	501
8.16	Lead-Acid Battery	502
8.16.1	Working Principle of Lead-Acid Cell	504
8.16.2	Maintenance of Lead-Acid Batteries	506
8.16.3	Applications of Lead-Acid Batteries	507
8.17	Alkaline Batteries	507
8.17.1	Nickel-Iron Alkaline Cell	507
8.17.2	Electrical Characteristics	508
8.17.3	Advantages and Disadvantages	508
8.18	Comparison Between Lead-Acid and Nickel-Iron Alkaline Cell	509
8.19	Nickel-Cadmium Cell	510

8.19.1	Working	511
8.19.2	Electrical Characteristics	511
8.19.3	Advantages and Disadvantages	511
8.20	Nickel-metal Hydride Battery	511
8.20.1	Construction	512
8.20.2	Cell Reactions	513
8.20.3	Features	513
8.20.4	General Characteristics	514
8.20.5	Self Discharge Characteristics	514
8.20.6	Recharging Characteristics	515
8.20.7	Safety Precautions	516
8.20.8	Applications	516
8.21	Zinc-carbon battery	516
8.21.1	Construction	516
8.21.2	Chemical Reactions	517
8.21.3	Applications	518
8.22	Dry Cell Battery	518
8.22.1	Applications	519
8.23	Lithium-ion battery	519
8.23.1	Construction	519
8.23.2	Electrochemistry	520
8.23.3	Applications	521
8.24	Capacity of A Battery	522
8.24.1	Factors Affecting Capacity of a Battery	523
8.25	Efficiency of A Battery	523
8.25.1	Solved Problems	524
8.26	Energy consumption	527
8.26.1	Solved Problems	527
8.27	Summary	528
8.28	Review Questions	528
8.29	Multiple Choice Questions	529