

# *Electrical Circuit Analysis*

## Authors

**Dr. V. Chandra Jagan Mohan**

Associate Professor

Department of EEE

Institute of Aeronautical Engineering College  
Dundigal, Hyderabad-500043

**Mr. T. Anil Kumar**

Assistant Professor

Department of EEE

Institute of Aeronautical Engineering College  
Dundigal, Hyderabad -500043



All rights reserved. No part of this publication which is material protected by this copyright notice may be reproduced or transmitted or utilized or stored in any form or by any means now known or hereinafter invented, electronic, digital or mechanical, including photocopying, scanning, recording or by any information storage or retrieval system, without prior written permission from the **Publisher**.

Information contained in this book has been published by **StudentsHelpline Publishing House (P) Ltd. , Hyderabad** and has been obtained by its Authors from sources believed to be reliable and are correct to the best of their knowledge. However, the Publisher and its Authors shall in no event be liable for any errors, omissions or damages arising out of use of this information and specifically disclaim any implied warranties or merchantability or fitness for any particular use.

**COPYRIGHT REGISTRATION DIARY NUMBER: 5606/2019-CO/L**

## **Seven Hills International Publishers, Hyderabad**

**A Part of StudentsHelpline Publishing House (P) Ltd.**

*(An ISO 9001 : 2015 Certified Company)*

### **Head Office**

# 326/C, III Floor, Surneni Nilayam

Near B K Guda Park, S R Nagar, Hyderabad - 500 038, INDIA

P.No:+91 40 23710657, 238000657 Fax: +91 40 23810657

### **Reg. Off**

# 5-68, Pedda Gorpadu, Pakala, Tirupati, Chittoor - 517 112 AP, INDIA

**mail:**studentshelpline.in@gmail.com

**www:**studentshelpline.org

## **© Seven Hills International Publishers, Hyderabad**

**First Edition-2019**

**ISBN 978-93-88096-14-0**

˘ **424/- Student Edition**

˘ **624/- Library Edition with HB**

*Printed at StudentsHelpline Group, S R Nagar, Hyderabad-38*

*Published by Surneni Mohan Naidu for Seven Hills International Publishers, Hyderabad - 38*

# *Electrical Circuit Analysis*

---

---

## **Module-I: Introduction to Electrical Circuits**

Circuit Concept: Basic definitions, Ohm's law at constant temperature, classifications of elements, R, L, C parameters, independent and dependent sources, Kirchhoff's laws, Equivalent Resistance of series, Parallel and series parallel networks.

Analysis of Electrical Circuits: Source Transformation, Star to Delta and Delta to Star transformation, Mesh analysis and Nodal analysis by Kirchhoff's laws, inspection method, super mesh, super node analysis.

## **Module-II: AC Circuits**

Single Phase AC Circuits: Representation of alternating quantities, Instantaneous, peak, RMS, average, form factor and peak factor for different periodic waveforms, phase and phase difference, 'j' notation, Concept of reactance, impedance, susceptance and admittance, rectangular and polar form. Concept of power, real, reactive, apparent power and complex power, power factor. Analysis of single phase AC Circuits consisting of R, L, C, RL, RC and RLC combinations.

## **Module-III: Magnetic Circuits and Network Theorems**

Faraday's laws of electromagnetic induction, concept of self and mutual inductance, dot convention, coefficient of coupling, composite magnetic circuit, analysis of series and parallel magnetic circuits, behaviors of series and parallel resonant networks.

Theorems: Zero Current Theorem, Tellegen's, Superposition, Reciprocity, Voltage Shift Theorem, Thevenin's, Norton's, Maximum power transfer and Milliman's and compensation theorems for DC excitations.

## **Module-IV: Solution of First and Second Order Networks**

Initial conditions, transient response of RL, RC and RLC series circuits with DC excitation, differential equation and Laplace transform approach.

## **Module-V: Two Port Network Parameters**

Two port network parameters: Z, Y, ABCD, hybrid and inverse hybrid parameters, conditions for symmetry and reciprocity, inter relationships of different parameters, interconnection (series, parallel and cascade) of two port networks, image parameters .

# *Electrical Circuit Analysis*

---

---

## **Chapter-I: Introduction to Electrical Circuits**

1.0	Objective and Outcomes x	2
1.1	Introduction	2
1.2	Circuit concept: Basic definitions	2
1.3	Electric Current	5
1.4	Electric Potential	7
1.5	Potential Difference	7
1.6	Voltage and E.M.F	8
1.7	Power	8
1.8	Ohm's Law at constant temperature	8
1.8.1	Limitations of Ohm's Law	9
1.8.2	Applications of Ohm's Law	10
1.8.3	Solved Problems	10
1.9	Classifications of Elements	13
1.10	R-L-C Parameters	14
1.10.1	Resistance (R)	14
1.10.2	Classification of Resistors	16
1.10.3	Colour Coding of Resistors	17
1.11	Inductor (L)	17
1.11.1	Classifications of Inductors	18
1.11.2	Specifications of Inductor	19
1.11.3	Conductivity	19
1.12	Concept of Capacitor	19
1.12.1	Classifications of Capacitors	21
1.12.2	Specifications of the Capacitor	21
1.12.3	Comparison of Active and Passive Components	22
1.12.4	Solved Problems	22
1.13	Standard symbols for electrical components	25
1.14	Fuse	27
1.14.1	Need	28
1.14.2	Rating	28
1.14.3	Requirements of a Fuse	29
1.14.4	Fusing Materials	29
1.14.5	Classification of Fuses	30
1.15	Voltage and Current Sources	32
1.16	Independent and Dependent Sources	34

1.16.1	Solved Problems	<b>36</b>
1.17	Kirchhoff's Laws	<b>37</b>
1.17.1	Solved Problems	<b>40</b>
1.18	Series Resistance	<b>43</b>
1.18.1	Equivalent Resistance for Series Connections	<b>44</b>
1.18.2	Voltage Divider Rule	<b>47</b>
1.18.3	Solved Problems	<b>48</b>
1.19	Resistance in Parallel	<b>52</b>
1.19.1	Characteristics of a Parallel Circuits	<b>54</b>
1.20	Series-Parallel Combination	<b>54</b>
1.21	Division of Current in Parallel Branch Circuit	<b>55</b>
1.21.1	Solved Problems	<b>58</b>
1.21.2	Comparison of Series and Parallel Circuits	<b>61</b>
1.22	Solved Problems on Series and Parallel Circuit	<b>61</b>
1.23	Summary	<b>73</b>
1.24	Review Questions	<b>73</b>
1.25	Multiple Choice Questions	<b>75</b>
<b>Chapter-II: Analysis of Electrical Circuits</b>		
2.0	Objective and Outcomes	<b>78</b>
2.1	Introduction	<b>78</b>
2.2	Source Transformation	<b>79</b>
2.2.1	Solved Problems	<b>80</b>
2.3	Star to Delta or Delta to Star Transformations	<b>84</b>
2.3.1	Delta-Star Transformation	<b>85</b>
2.3.2	Star-Delta Transformation	<b>87</b>
2.3.3	Conversion of Delta into Equivalent Star	<b>89</b>
2.3.4	Conversion of Star into Equivalent Delta	<b>89</b>
2.3.5	Solved Problems	<b>91</b>
2.4	Mesh Analysis by Kirchhoff's laws	<b>104</b>
2.5	Node Analysis by Kirchhoff's laws	<b>116</b>
2.5.1	Concept of Nodal Analysis	<b>117</b>
2.5.2	Nodal Analysis Illustration	<b>117</b>
2.5.3	Solved Problems	<b>118</b>
2.6	Inspection Method	<b>128</b>
2.6.1	Solved Problems	<b>129</b>
2.6.2	Nodal Equations by Inspection Method	<b>130</b>
2.6.3	Solved Problems	<b>131</b>
2.7	Super Mmesh for DC Excitations	<b>132</b>
2.7.1	Solved Problems	<b>135</b>
2.8	Super node for DC Excitations	<b>137</b>
2.8.1	Solved Problems	<b>138</b>

2.9	Comparison of Mesh and Nodal Analysis	140
2.10	Summary	141
2.11	Review Questions	142
2.12	Multiple Choice Questions	144

### Chapter-III: AC Circuits

3.0	Objective and Outcomes	148
3.1	Introduction	148
3.2	Important Definitions	148
3.3	Comparison of Alternating Current and Direct Current	152
3.4	The sinusoidal waveform	152
3.4.1	Significance of Sine Wave	154
3.4.2	Different Forms of E.M.F Equation	154
3.5	Representation of Alternating Quantities	154
3.5.1	Instantaneous Values	154
3.5.2	RMS (or) Virtual (or) Effective Value of AC	155
3.5.3	Average (or) Mean Value of AC	157
3.5.4	Form Factor	158
3.5.5	Peak Factor	159
3.5.6	Peak Value (or) Time Period of A.C	159
3.5.7	Solved Problems	160
3.6	Phase relations	164
3.6.1	Phase	164
3.6.2	Phase Difference	165
3.6.3	Solved Problems	167
3.7	Representation of an AC Quantity by a Rotating Vector	167
3.8	J-operator (or) J Notation	169
3.8.1	Solved Problems	171
3.9	Polar and rectangular form of Complex Numbers	171
3.10	Phasor Algebra	172
3.11	Impedance Complex Number	173
3.12	Admittance of Complex Number	174
3.13	Concept of reactance	175
3.14	Impedance	176
3.15	Susceptance	177
3.16	Admittance	177
3.17	Mathematical Representation of Phasors	178
3.18	Solved Problems	180
3.19	Concept of Real, Reactive Power	183
3.20	Apparent Power and Complex Power	184
3.21	Power Factor	186
3.21.1	Solved Problems	187

3.22	AC Circuit	188
3.22.1	AC Through Pure Resistance	188
3.22.2	AC Through Pure Inductance	189
3.22.3	AC Through Capacitance	190
3.23	Representation of AC Series Circuits	191
3.23.1	RL Series Circuit	191
3.23.2	RC Series Circuit	193
3.23.3	RLC Series Circuit	195
3.24	Representation Parallel AC Circuits	198
3.24.1	RL Parallel Circuit	198
3.24.2	RC Parallel Circuit	199
3.24.3	RLC Parallel Circuit	200
3.25	Solved Problems	201
3.26	Advantages of Alternating Current over Direct Current	210
3.27	Disadvantages of A.C over D.C	210
3.28	Summary	211
3.29	Review Questions	211
3.30	Multiple Choice Questions	213
<b>Chapter-IV: Magnetic Circuits</b>		
4.0	Objectives	218
4.1	Introduction	218
4.2	Magmetic Circuit	218
4.3	Important Definitions	221
4.3.1	Solved Examples	226
4.4	Electromagnetic Induction	229
4.5	Faraday's Law of Electromagnetic Induction	230
4.5.1	Faraday's First Law	231
4.5.2	Faraday's Second Law	231
4.5.3	Applications of Faraday's Law	231
4.5.4	Integral Form of Faraday's Law	232
4.5.5	Differential Form of Faraday's Law	232
4.5.6	Solved Examples	233
4.6	Direction of Induced E.M.F. and Current	237
4.6.1	Lenz's Law	237
4.6.2	Fleming's Right Hand Rule	238
4.6.3	Fleming's Left-Hand Rule	239
4.7	Induced E.M.F	240
4.7.1	Dynamically Induced E.M.F	240
4.7.2	Statically Induced E.M.F	241
4.8	Motional Electromotive Force	244

4.9	Time Varying Magnetic Fields	244
4.10	Self and Mutual Inductance	246
	4.10.1 Self Inductance	246
	4.10.2 Mutual Inductance	246
	4.10.3 Solved Example	248
4.11	Dot Convention	253
	4.11.1 Solved Problems	256
4.12	Co-efficient of Coupling	257
	4.12.1 Solved Problems	259
4.13	Composite Magnetic Circuit	263
4.14	Analysis of Series and Parallel Magnetic Circuits	265
	4.14.1 Analysis of Series Magnetic Circuits	266
	4.14.2 Analysis of Parallel Magnetic Circuits	267
	4.14.3 Magnetic Leakage (or) Leakage Flux	268
	4.14.4 Solved Examples	269
4.15	Comparison between Magnetic and Electric Circuits	283
4.16	Resonance	285
	4.16.1 Resonance in Series circuit	285
	4.16.2 Parallel Resonance in RLC Circuit	290
	4.16.3 Q - Factor, Selectivity and bandwidth	294
	4.16.4 Selectivity, Bandwidth and Q-factor of a Series Circuit	294
	4.16.5 Selectivity, Bandwidth and Q-factor of Parallel Resonant Circuit	297
	4.16.6 Compare Series and Parallel Resonance Circuits	299
	4.16.7 Solved Problems	299
4.17	Summary	309
4.18	Review Questions	310
4.19	Objective Questions	312
<b>Chapter-V: Network Theorems</b>		
5.0	Objective and Outcomes	318
5.1	Introduction	318
5.2	Tellegen's Theorem	318
	5.2.1 Solved Problems	320
5.3	Superposition Theorem	324
	5.3.1 Solved Problems	326
5.4	Reciprocity Theorem	342
	5.4.1 Solved Problems	344
5.5	Thevenin's Theorem	354
	5.5.1 Solved Problems	357
5.6	Norton's Theorem	369
	5.6.1 Solved Problems	371
5.7	Maximum Power Transfer Theorem	385



5.7.1	Solved Problems	386
5.8	Milliman Theorem	394
5.8.1	Solved Problems	396
5.9	Compensation Theorem	399
5.9.1	Solved Problems	401
5.10	Summary	406
5.11	Review Questions	407
5.12	Multiple Choice Questions	410

**Chapter-VI: Solution of First and Second Order Networks**

6.0	Objectives	416
6.1	Introduction	416
6.2	Important Definitions	416
6.3	Transient Response	417
6.4	The Voltage and Current Relationships for Impulse, Step and Ramp Functions	418
6.5	Initial Conditions	420
6.5.1	Procedure for Evaluating Initial Conditions	423
6.5.2	Solved Examples	424
6.6	Transient Response of RL Circuit	427
6.6.1	Solved Examples	430
6.7	Transient Response of RC Circuit	435
6.8	Transient Response of RLC Circuit	439
6.8.1	Solved Examples	441
6.9	Differential Equations of First-order Networks	449
6.9.1	Initial Conditions	449
6.9.2	Final Conditions	451
6.10	Laplace Transformation	451
6.11	Properties of Laplace Transform	453
6.12	Useful Laplace Transforms	455
6.13	Steps to find Transient Response using Laplace Transform	456
6.14	Circuit Elements in the s-Domain	456
6.14.1	Resistor in the s-Domain	456
6.14.2	Inductor in s-Domain	456
6.14.3	Capacitor in s-Domain	457
6.15	DC Response of RC Series Circuit	458
6.15.1	Solved Examples	459
6.16	DC Response of R-L Series Circuit	461
6.16.1	Solved Examples	463
6.17	DC Response of An R-L-C Series Circuit	467
6.17.1	Solved Examples	468
6.18	Summary	472

6.19	Review Questions	<b>473</b>
6.20	Multiple Choich Questions	<b>475</b>
<b>Chapter-VII: Two Port Network Parameters</b>		
7.0	Objectives	<b>480</b>
7.1	Introduction	<b>480</b>
7.2	Two Port Network Parameters	<b>480</b>
7.3	Z-parameters (Impedance Parameters)	<b>481</b>
7.3.1	Solved Examples	<b>483</b>
7.4	Y-parameters (Admittance Parameters)	<b>488</b>
7.4.1	Solved Examples	<b>490</b>
7.5	Abcd-parameters (Transmission Parameters)	<b>495</b>
7.5.1	Solved Examples	<b>496</b>
7.6	Hybrid Parameters (H-parameters)	<b>502</b>
7.6.1	Solved Examples	<b>503</b>
7.7	Inverse Hybrid Parameters or G- Parameters	<b>509</b>
7.8	Inter Relationships of Different Parameters	<b>510</b>
7.8.1	Relationship between Z and Y parameters	<b>510</b>
7.8.2	Relationship between Y and h parameters	<b>512</b>
7.8.3	Relationship between ABCD and h parameters	<b>512</b>
7.8.4	Relationship between Z and h parameters	<b>512</b>
7.8.5	Relationship between Z and ABCD parameters	<b>513</b>
7.8.6	Relationship between Y and ABCD parameters	<b>514</b>
7.8.7	Conversion of Parameters	<b>514</b>
7.8.8	Solved Examples	<b>515</b>
7.9	Conditions for Symmetry and Reciprocity	<b>525</b>
7.9.1	Reciprocity and Symmetry in Z-parameter Representation	<b>525</b>
7.9.2	Reciprocity and symmetry in Y parameter represen-tation	<b>526</b>
7.9.3	Reciprocity and Symmetry in ABCD parameter representation	<b>527</b>
7.9.4	Reciprocity and Symmetry in h-Parameter Representation	<b>528</b>
7.9.5	Solved Examples	<b>529</b>
7.10	Interconnection (series, parallel and cascade) of two port networks	<b>536</b>
7.10.1	Series interconnection of two port network	<b>537</b>
7.10.2	Parallel connection of two port net work	<b>538</b>
7.10.3	Cascade Connection of Two Port Networks	<b>539</b>
7.10.4	Solved Examples	<b>540</b>
7.11	Image Parameters	<b>548</b>
7.12	Solved Examples	<b>551</b>
7.13	Summary	<b>552</b>
7.14	Review Questions	<b>552</b>
7.14	Multiple Choice Questions	<b>555</b>